

ECE 368, Fall 2006, Instructor: Prof. Shantanu Dutt

Midterm Exam: Fri., Nov. 10, Time: 1:30-2:50 pm

Exam Format: Open Book (only text book and one sheet of notes), Total Points: 100

Important Note: (1) Write your name on the top of this question sheet and submit along with your answer book. (2) You need to show all your work **clearly** in deriving the answers. Just writing down the final answers is not enough.

Suggestion: Begin by reading all questions and do those first that you think you know best.

1. Regular Circuit Description using Generate Statements

(a) You need to design an 8-bit equality comparator which outputs a 1 when both its input numbers X and Y are equal. Otherwise it outputs a 0. The comparator delay needs to be small, in particular, sublinear in the number of bits n of the input numbers for the general n -bit version of your design. Draw the circuit for your 8-bit comparator using only 2-input gates of one or more of the following types: and, or, xor, xnor. Assuming a delay of t_d for a 2-input gate, derive the delay for your 8-input equality comparator as well as its n -input version (assume $n = 2^k$ for some k). **25**

Hint: Use the associativity property of part of the equality-comparison computation to design a tree-structured circuit. You may need more than one gate type.

(b) Give a structural VHDL description of the general n -bit version of your above design assuming $n = 2^k$, and make k a generic parameter. Assume availability of entity-architectures for 2-input gates of the above types. Another generic parameter should be t_d which is the delay desired for the 2-input gates used as components in your VHDL description. The design should be described using generate statements. An example 2-input OR gate entity description is given below and you can assume similar entity descriptions of whatever 2-input gates you need to use. **25**


```
entity or2 is
generic (td: time := 4 ns); -- propagation delay of gate
port (a, b : in std_logic; c: out std_logic);
end entity or2;
```

The entity description of your equality-comparator circuit should be:

```
entity eq_comp is
generic (k: natural; td: time); -- there are  $n = 2^k$  bits in each input  $X, Y$ 
port (X, Y: in std_logic_vector(2**k - 1 downto 0);
f: out std_logic -- circuit output);
end entity eq_comp;
```

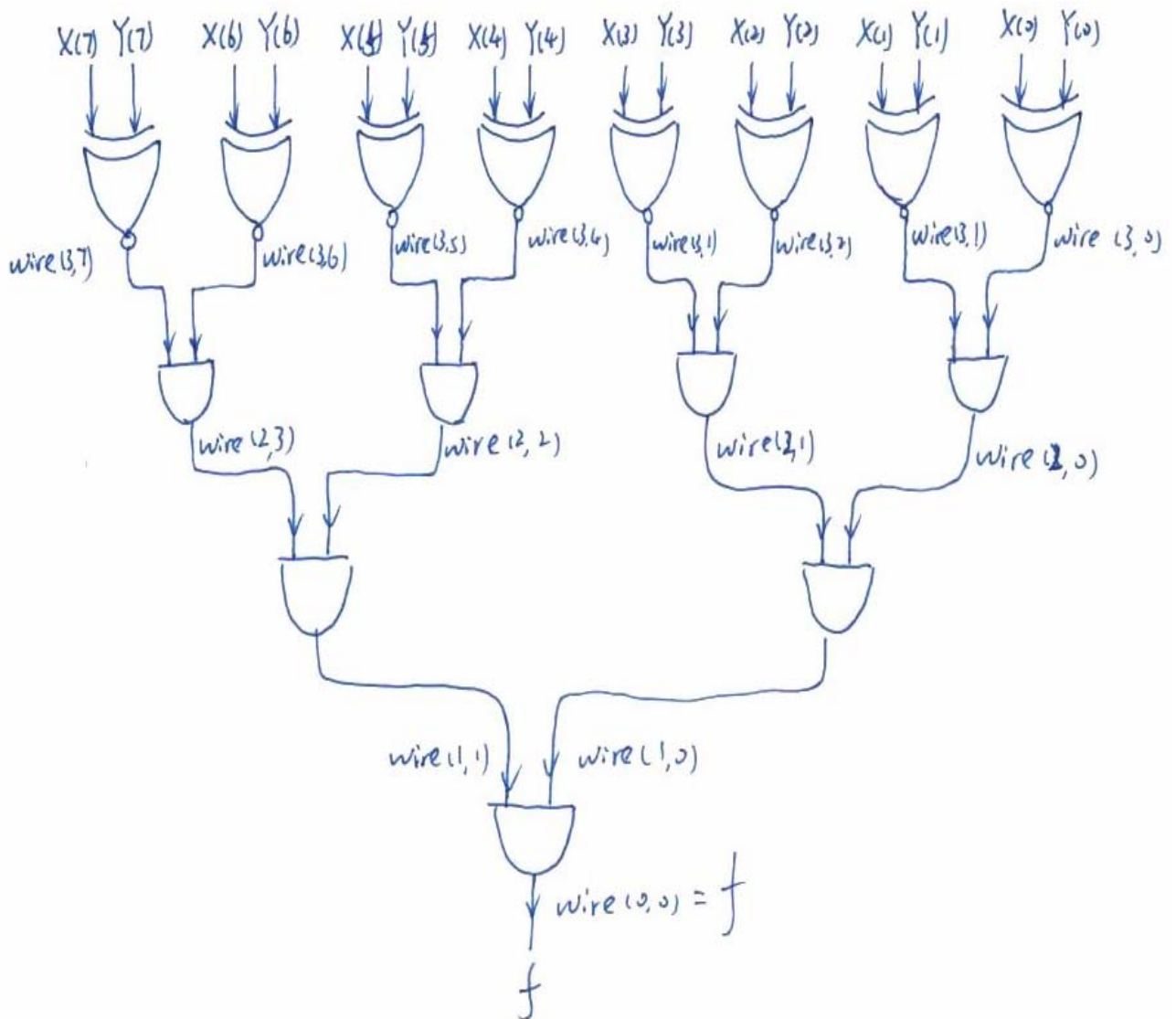1. Regular Circuit Description using Generate Statements

(a): The idea is: if and only if all 8 bits of X, Y are the same, then the output can be 1. We can use a 2-input xnor gate to determine whether two 1-bit is equal or not. If equal, output 1, otherwise, output 0. Now that we get 8 outputs of the 8 2-input xnor gate, if any one is 0, then the final output of the circuit is 0 which means not equal. Obviously, we should use 2-input and gate to make this judgment. The tree circuit is as followed:



Concerning n-input version, there will be k+1 levels. So the delay of n-input version is $2 \cdot (k+1)$ ns. Thus the delay of 8-input equality comparator should be 8 ns.

At the first level, we need n 2-input xnor gates. At the following levels, only 2-input and gates are needed. The number a of the 2-input and gates are:

$$a = 1 + 2 + 4 + \dots + 2^{k-1} = 2^k - 1;$$

(b) VHDL CODE:

```
Library IEEE;
```

```
use IEEE.STD_LOGIC_1164.all;
```

```
use IEEE.std_logic_arith.all;
```

```
entity eq_comp is
```

```
generic (k: natural; td : time); -- there are  $n = 2^{*k}$  bits in each input X, Y
```

```
port (X, Y : in std_logic_vector( $2^{*k} - 1$  downto 0);
```

```
      f : out std_logic); -- circuit output
```

```
end eq_comp;
```

```
architecture structural of eq_comp is
```

```
component and2 is
```

```
generic (td : time := 4 ns); -- propagation delay of gate
```

```
port (a, b : in std_logic;
```

```
      c: out std_logic);
```

```
end component;
```

```
component xnor2 is
```

```
generic (td : time := 4 ns); --propagation delay of gate
```

```
port (a, b : in std_logic;
```

```
      c: out std_logic);
```

```
end component;
```

```
type matrix is array (k downto 0,  $2^{*k} - 1$  downto 0) of std_logic;
```

```
signal wire: matrix;
```

```
begin
```

```
  outer_loop: for j in k downto 0 generate
```

```
    inner_loop: for i in 0 to  $2^{*j}-1$  generate
```

```
      first_level: if j = k generate
```

```
        xnor2_gate: xnor2 generic map (td) port map(X(i), Y(i), wire(j, i));
```

```
        end generate;
```

```
      next_level: if j < k generate
```

```
        and2_gate: and2 generic map (td) port map(wire(j+1,  $2^{*i}$ ), wire(j+1,  $2^{*i}+1$ ),
```

```
        wire(j, i));
```

```
        end generate;
```

```
      end generate;
```

```
    end generate;
```

```
  f <= wire(0,0);
```

```
end architecture structural;
```

2. FSM Design

Design a Moore FSM equality comparator with 2 1-bit serial input lines x, y . The FSM is supposed to determine the equality or non-equality of every disjoint (non-overlapping) group of 5 bits obtained on the x, y lines. If it detects equality of the current group of 5 bits, it should output a 1 for 3 ccs on its output line f . Assume that new bits on the x, y lines are available every clock cycle.

Remember to label the reset state as such. The example below gives 3 groups of 5 bits and what the output should be. Note that a 1 output on the f line naturally appears (i.e., you do not have to explicitly design for it) 1cc after the appearance of the 5th bits of two equal 5-bit numbers, and the example below shows that.

x bits	0	1	1	0	1	0	1	1	1	0	0	0	1	0	1	$0 \dots$
y bits	0	1	1	0	1	1	1	1	0	0	0	0	1	0	1	$0 \dots$
f	0	0	0	0	0	1	1	1	0	0	0	0	0	0	0	$1 \dots$

Note that the difference between the equality comparator in Problem 1 and the equality comparator for this problem, is that the Problem 1 comparator has all n input bits available simultaneously, and hence it can be a combinational circuit, whereas in this problem the bits are available serially (one after the other on the same line) and hence the comparator has to be a sequential circuit (FSM) since it has to “remember” the previous bits.


2. FSM Design

The FSM is supposed to determine the equality of every disjoint (non-overlapping) group of 5 bits obtained on the x, y lines. So it has to “remember” the previous bits, in other word, each bit of the disjoint 5-bit group need to have a state.

If we detect that the i_{th} bit of x and y are not equal, x and y are not equal. So we can ignore the following bits of x and y and safely output 0. For example, if we detect the 1th bits of x and y are not equal, then the following 4 states outputs are all 0 regardless of their value.

If the FSM detects equality of the current group of 5 bits, it required 3 ccs high output. As we have done in the lab, we need 4 other analog states which are the same as the originals except the output is 1.

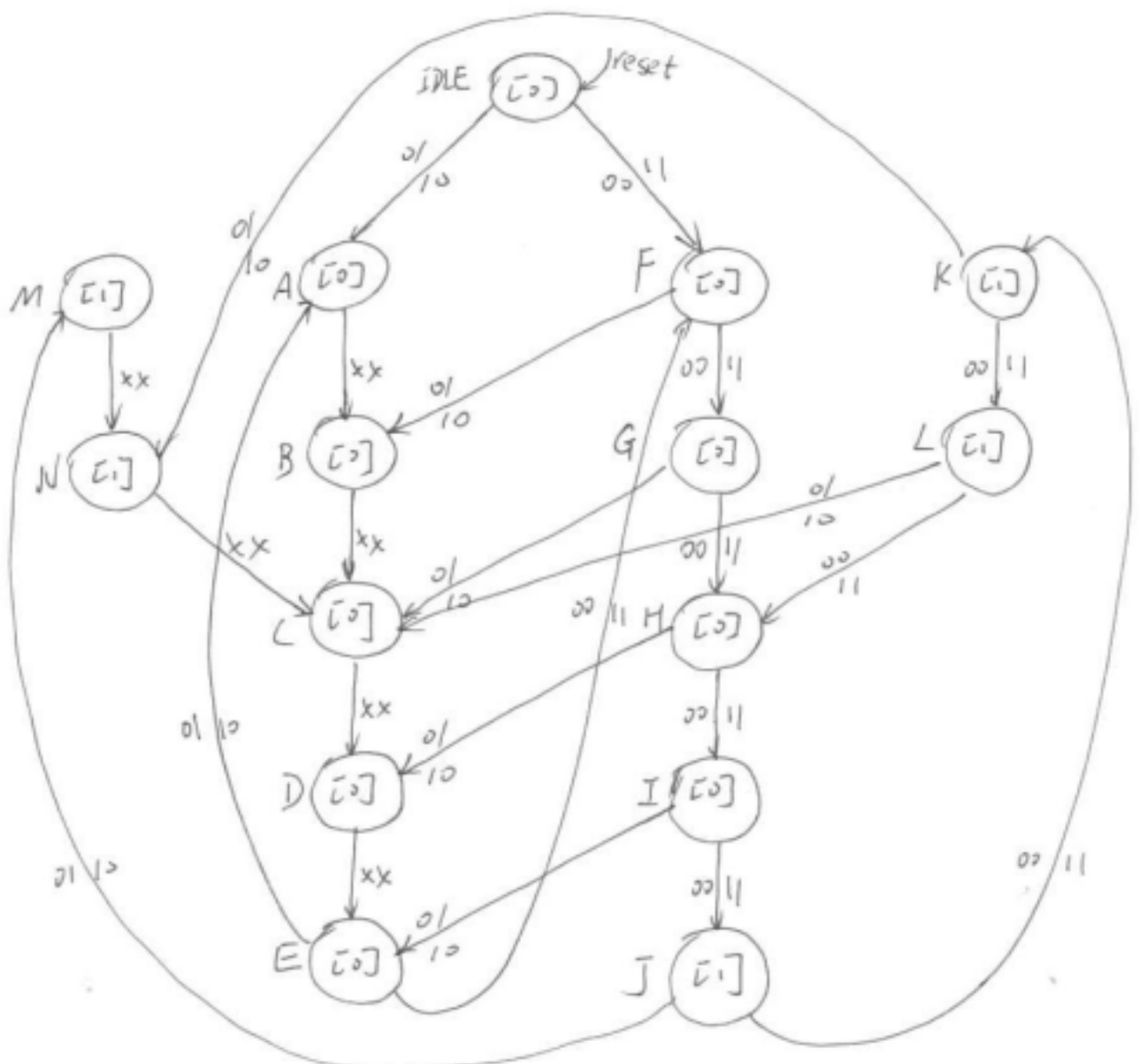The FSM diagram is as followed (00/11 stands for 1 bit of x and y equal, 01/10 stands for 1 bit of x and y not equal, xx stands for don't care):



The VHDL code is:

```
Library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity fsm_eq_comp is
    port (x, y, clk, reset: in std_logic;
          fout: out std_logic);
end entity fsm_eq_comp;

architecture behav of fsm_eq_comp is

    type states is (IDLE, A, B, C, D, E, F, G, H, I, J, K, L, M, N);
    signal next_state, curr_state: states:=IDle;

begin

    ff_proc: process is          -- 2 ns delay
    begin
        wait until (clk'event and clk='1') or (reset='1');
        if reset='1' then
            curr_state <= IDLE after 2 ns;
        else
            curr_state <= next_state after 2 ns;
        end if;
    end process ff_proc;

    op_proc: process (curr_state) is    -- 3 ns delay
    begin

        case curr_state is
            when IDLE => fout <= '0' after 3 ns;
            when A => fout <= '0' after 3 ns;
            when B => fout <= '0' after 3 ns;
            when C => fout <= '0' after 3 ns;
            when D => fout <= '0' after 3 ns;
            when E => fout <= '0' after 3 ns;
            when F => fout <= '0' after 3 ns;
            when G => fout <= '0' after 3 ns;
            when H => fout <= '0' after 3 ns;
            when I => fout <= '0' after 3 ns;
            when J => fout <= '1' after 3 ns;
```

```

    when K => fout <= '1' after 3 ns;
    when L => fout <= '1' after 3 ns;
    when M => fout <= '1' after 3 ns;
    when N => fout <= '1' after 3 ns;
end case;

end process op_proc;

ns_proc: process (curr_state,x, y) is    --5 ns delay
begin

case curr_state is
    when IDLE=>
        if ((x='1' and y = '0') or (x = '0' and y = '1')) then
            next_state <= A after 5 ns;
        else
            next_state <= F after 5 ns;
        end if;
    when A=>
        next_state <= B;
    when B=>
        next_state <= C;
    when C=>
        next_state <= D;
    when D=>
        next_state <= E;
    when E=>
        if ((x='1' and y = '0') or (x = '0' and y = '1')) then
            next_state <= A after 5 ns;
        else
            next_state <= F after 5 ns;
        end if;
    when F=>
        if ((x='1' and y = '1') or (x = '0' and y = '0')) then
            next_state <= G after 5 ns;
        else
            next_state <= B after 5 ns;
        end if;
    when G=>
        if ((x='1' and y = '1') or (x = '0' and y = '0')) then
            next_state <= H after 5 ns;
        else
            next_state <= C after 5 ns;
        end if;

```

```

when H=>
    if ((x='1' and y = '1') or (x = '0' and y = '0')) then
        next_state <= I after 5 ns;
    else
        next_state <= D after 5 ns;
    end if;
when I=>
    if ((x='1' and y = '1') or (x = '0' and y = '0')) then
        next_state <= J after 5 ns;
    else
        next_state <= E after 5 ns;
    end if;
when J=>
    if ((x='1' and y = '1') or (x = '0' and y = '0')) then
        next_state <= K after 5 ns;
    else
        next_state <= M after 5 ns;
    end if;
when K=>
    if ((x='1' and y = '1') or (x = '0' and y = '0')) then
        next_state <= L after 5 ns;
    else
        next_state <= N after 5 ns;
    end if;
when L=>
    if ((x='1' and y = '1') or (x = '0' and y = '0')) then
        next_state <= H after 5 ns;
    else
        next_state <= C after 5 ns;
    end if;
when M=>
    next_state <= N;
when N=>
    next_state <= C;
end case;
end process ns_proc;
end architecture behav;

```

3. VHDL: Signals and Variables

Consider the following architecture description.

```
architecture XYZ of ABC is
signal a, b, c, d: integer := 1;
signal clk: bit := '1';
begin

clock: process is
begin
clk <= '1','0' after 4 ns;
wait for 8 ns ;
end process clock;

foo: process is
variable x, y, z: integer := 1;
begin
-- point 1
x := y + 2*(b**3);
a <= b**2 + x;
b <= a**2 + y after 4 ns;
--point 2
wait for 2 ns;
--point 3
c <= a+b;
y := 2*a + c;
--point 4
wait until clk'event and clk='1';
d <= a + b + c;
--point 5
wait on clk;
end process foo;
end architecture XYZ;
```

Determine the simulation time, and values of the signals and variables at the following points and iterations given in the table below. Assume that simulation begins at time 0 and that the first value of the clock is '1' (and thus that the first transition on the clock will be negative edge and will occur at time 4 ns—half the clock period).

25

iter 1, point 1	time	a	b	c	d	x	y	z
iter 1, point 2	time	a	b	x				
iter 1, point 3	time	a	b	x				
iter 1, point 4	time	b	c	y				
iter 1, point 5	time	b	c	d				
iter 2, point 1	time	a	b	c	d	x	y	z
iter 2, point 2	time	a	b	x				

3. VHDL: Signals and Variables

Variable assignment: the value of the variable will immediately change.

Signal assignment: the value of signals will not change immediately, but after Δ time, which is smaller than any real time;

iter 1, point 1:

At the very beginning, time is 0;

a, b, c, d, x, y, z are the original values which are all 1s.

iter 1, point 2:

Variable and signal assignments cannot advance simulation time, so time is 0;

x is a variable, so x changes immediately, $x = 1 + 2 * (1 ** 2) = 3$;

a, b are signals, so they will not change immediately, so $a = 1$, $b = 1$;

a will change after Δ and it will use the new value of x (3);

b will change after 4 ns and it will use the old value of a (1) because a doesn't change at current time;

iter 1, point 3:

wait for statement will advance simulation time, so time is 2 ns now!

Now the value of a changes. $a = 1 ** 2 + 3 = 4$;

x will not change, so x is still 3;

The current time is 2 ns, so b haven't changed and its value is 1.

iter 1, point 4:

variable and signal assignment cannot advance simulation time, so time is 2 ns;

b doesn't change so $b = 1$;


c will change after Δ so now c is still 1; c will use the new value of a (4) and old value of b (1);

y will change immediately. Here a is 4, c is the old value 1 as c haven't changed yet.

So $y = 2 * 4 + 1 = 9$;

iter 1, point 5:

 wait until statement will advance the simulation time. The waveform of the clk should be like this:



so the first positive edge of clk will come at 8 ns, thus the current time is 8 ns;

The value of b will change to 2, $b = 1^{**}2 + 1 = 2$;

c will take effect which $c = 4+1 = 5$;

d will not change immediately, so d is still 1;

The “wait on clk;” statement will advance the simulation time to 12 ns as clk will change at 12 ns;

Now d will change to $a+b+c = 4+2+5=11$;

iter 2, point 1:

the current time should be 12 ns;

Given the above result: $a = 4, b = 2, c = 5, d = 11, x = 3, y = 9, z = 1$;

iter2, point 2:

use the same analysis given in iter1, point 2.

time = 12 ns;

Now $x = 25$; a, b will not change: $a = 4, b = 2$;

So the answer is as followed:

iter 1, point 1	time	a	b	c	d	x	y	z
	0 ns	1	1	1	1	1	1	1
iter 1, point 2	time	a	b	x				
	0 ns	1	1	3				
iter 1, point 3	time	a	b	x				
	2 ns	4	1	3				
iter 1, point 4	time	b	c	y				
	2 ns	1	1	9				
iter 1, point 5	time	b	c	d				
	8 ns	2	5	1				
iter 2, point 1	time	a	b	c	d	x	y	z
	12 ns	4	2	5	11	3	9	1
iter 1, point 2	time	a	b	x				
	12 ns	4	2	25				