

ECE 465 Quiz 1: Solution

Prob. 1

Q: Consider the function $f(a,b,c,d) = \sum_m (2,3,6,7,9,13,14,15)$. Give the formal definition of (a) a *minterm*, (b) a *prime implicate*, (c) an *implicant*, and (d) *covering of one implicant by another*

AND

Illustrate the definition using a K-map, stating the product/sum term(s) corresponding to the examples of each of the above definitions in the K-map.



Soln:

Minterm: a product of literals (complemented or uncomplemented form) containing each variable of the function exactly once.

Prime Implicate: On a K-map, a prime implicate is a group of adjacent maxterms that is not covered by a larger group of maxterm.

Implicant is a product term which covers minterms of a function. i.e. if g is an implicant of function f and if $g=1$ then $f=1$. So, an implicant covers one or more minterms of f .

Covering of one implicant by another if g_1 and g_2 are implicants of function f and g_1 covers g_2 then it means that g_1 is a superset of g_2 .

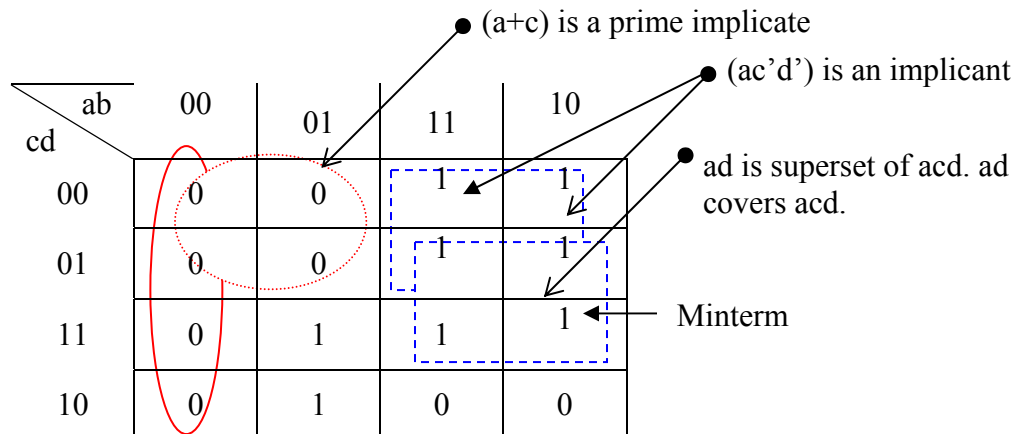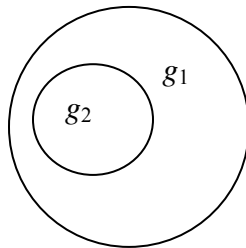

Prob. 2

Q: Let f be a function with an implicant g and an implicate h . What can you say about the value of f when: (a) $g=1$; (b) $h=1$; (c) $g=0$; and (d) $h=0$?

Soln:

(a) $g=1 \rightarrow f=1$

(b) $h=1 \rightarrow f$ depends on other implicates (if h is the only implicate, only then is f definitely 1)

(c) $g=0 \rightarrow f$ depends on other implicants (if g is the only implicant, only then is f definitely 0)

(d) $h=0 \rightarrow f=0$


Prob. 3

Q: The consensus theorem is stated as:

$$xy + \bar{y}z + xz = xy + \bar{y}z$$

Prove the consensus theorem using a K-map. Besides showing the necessary prime implicants grouping in the K-map, also state clearly in words how the K-map with the above prime implicants proves the theorem.

Soln:

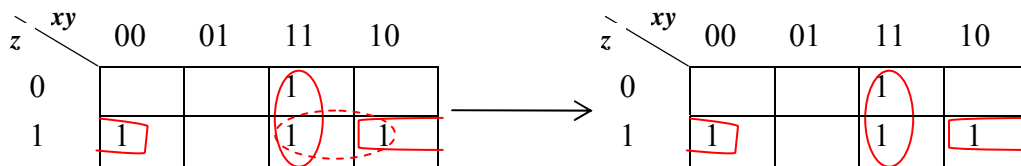

All 3 Prime Implicants (PIs) $xy, \bar{y}z, xz$.
The consensus xz of the other 2 PIs is shown with a dashed oval.

The consensus xz is not needed in the minimized expression as its minterms (MTs) are covered by the 2 PIs ($xy, \bar{y}z$) of which it is a consensus

Prob. 4

Q: (a) Consider a 3-bit number X . Provide a TT for the output number $Z = \text{int}(\sqrt{X})$, where $\text{int}(y)$, is the integer portion of a real number y . Note that Z can be a multi-bit number.

(b) You need to give a 2-level NOR-gate circuit for Z . For this purpose either obtain a minimized SOP or minimized POS expression for each bit of Z using a K-map (whichever you think is more convenient for an implementation using only NOR gates) and then obtain the NOR-gate circuit using this minimized expression.

Assume that NOR gates with any number of inputs that you need are available, and that all variables and their complemented forms (i.e., all *literals*) are available.

Soln:

X			Z	
x_2	x_1	x_0	z_1	z_0
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	0	1
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

Generate POS, $z_0 = \prod_M(0,4,5,6,7) = x_2' (x_1 + x_0)$ after simplification using K-map
 $z_1 = \prod_M(0,1,2,3) = x_2$

