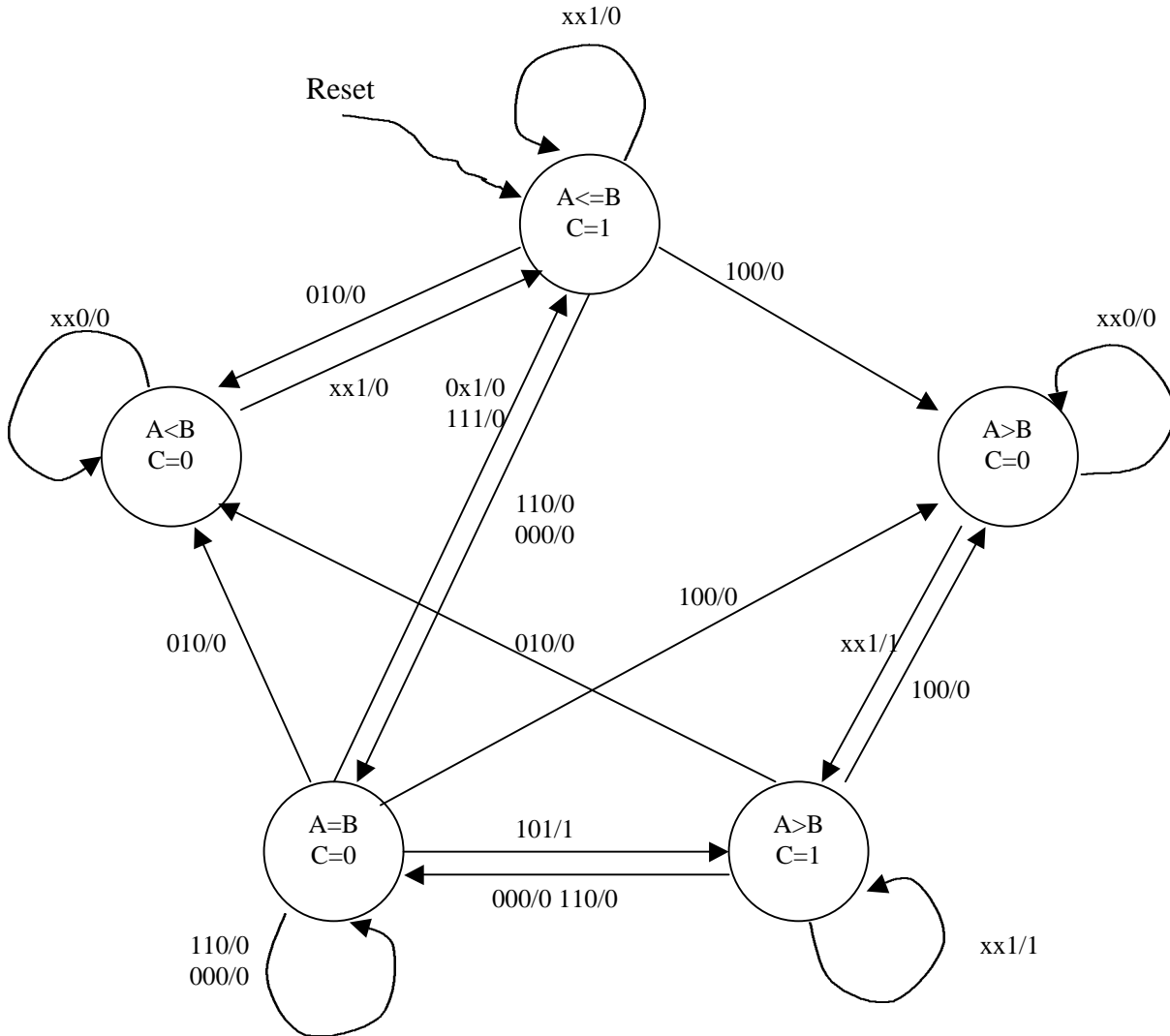


Solution of Sample Final

1. FSM Design



2. Timing Methodology

Other parameter are as same as those in the HW6

Margin = 1.1

$T_{skew} = 5ns$

$Max(T_{p,FF}) = 40ns$

$Max(T_{p,Logic}) = 20 \times 2 = 40ns$ (NAND-NAND Implementation)

$T_{SU} = 20ns$

Assume Φ_1 is the clock for the slave and Φ_2 for the master FFs

$$\begin{aligned} T_{\Phi_1-\Phi_2} &= \text{margin}[\max(T_{p,FF}) + T_{SU} + T_{Skew} + \max(T_{p,Logic})] \\ &= 1.1[40+20+5+40] \\ &= 115.5 \text{ ns} \end{aligned}$$

$$T_{\Phi_2-\Phi_1} = \text{margin}[\max(T_{p,FF}) + T_{SU} + T_{Skew}] < T_{\Phi_1-\Phi_2}$$

For Symmetric clock design, $T_{\Phi_1-\Phi_2}$ and $T_{\Phi_2-\Phi_1}$ have to be equal, so $T_{\Phi_2-\Phi_1} = 115.5 \text{ ns}$

$$T_{CLK_1} = 2 \max(T_{\Phi_1-\Phi_2}, T_{\Phi_2-\Phi_1}) = 2T_{\Phi_1-\Phi_2} = 2 * 115.5 = 231 \text{ ns}$$

3. Moore Machine

(a) $2^{N_{FF}-1} < N_S \leq 2^{N_{FF}}$
 $N_{FF} = 4$

The minimum number of states in the state-transition diagram is $2^3 + 1 = 9$.

The maximum number of states in the state-transition diagram is $2^4 = 16$.

(b) 3 input bits

The minimum number of Transition arrows starting at a particular state is 1.

The maximum number of Transition arrows starting at a particular state is $2^3 = 8$.

(c) The minimum number of Transition arrows that can end at a particular state is 1, because no state is isolated.

All possible transition arrows are 16 (# of max states) \times 8 (# of max input) = 128 . And since no state is isolated, every state needs at least 1 input. So the maximum number of transition arrow that can end at a particular state is $16 \times 8 - 15 = 113$.

(d) 7 output bits

The minimum number of different binary patterns that can be displayed on the outputs is **2**, otherwise if only 1 output, the machine does not do anything useful.

Since this is a Moore machine, one output is associated with each state. The max # of different output = $\min(2^7, \text{max \# of states}) = (2^7, 16) = 16$.

4. State Minimization

X

	0	1
S ₀	S ₁ /0	S ₄ /0
S ₁	S ₂ /0	S ₁ /0
S ₂	S ₁ /0	S ₆ /0
S ₃	S ₁ /0	S ₃ /0
S ₄	S ₅ /0	S ₄ /0
S ₅	S ₂ /0	S ₁ /0
S ₆	S ₅ /0	S ₃ /1


S ₁	S₁S₂ S₁S₄					
S ₂	S₄S₆	S₁S₆				
S ₃	S₄S₃ ✓	S₁S₂	S₃S₆			
S ₄	S₁S₅ ✓	S₂S₆	S₁S₅ S₄S₆	S₁S₅ ✓		
S ₅	S₁S₄ S₁S₂	✓	S₁S₂ S₁S₆	S₁S₂ S₁S₃	S₁S₄ S₂S₃	
S ₆	X	X	X	X	X	X
	S ₀	S ₁	S ₂	S ₃	S ₄	S ₅

From above table, we get the reduced state as following,

(S₀S₃S₄) (S₁S₅)(S₂) (S₆)
A' B' C' D'

X

	0	1
A'	B'/0	A'/0
B'	C'/0	B'/0
C'	B'/0	D'/0
D'	B'/0	A'/1

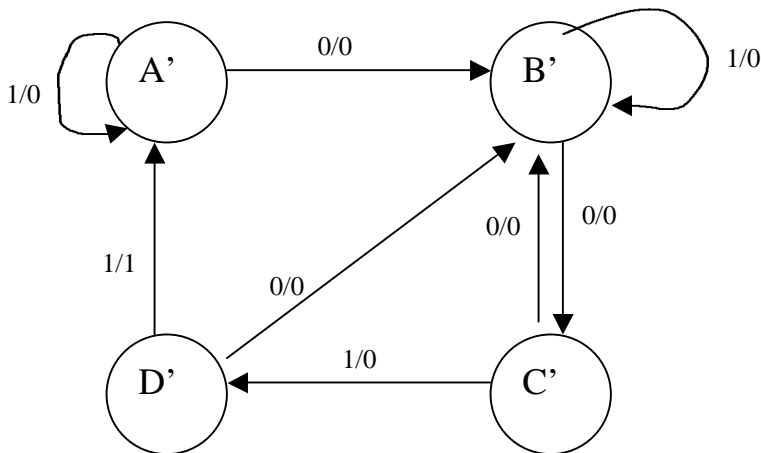

5. Testing

$$F^{p/d} = f^{p/d} \oplus f = 0$$

$F^{p/d}$ represents all tests for fault p/d

- $F^{p/d} = 0$. No test is available for the fault $f^{p/d}$. $f^{p/d}$ is untestable
- $F^{p/d} = 1$. Any input combination can be used as a test for fault $f^{p/d}$
- No

6. Testing

$$f = \overline{\overline{x_1 x_2 + x_3 x_4 + x_5 x_6}} = x_1 x_2 \cdot \overline{x_3 x_4} \cdot x_4 x_5 = x_1 x_2 (\overline{x_3} + \overline{x_4}) x_4 x_5$$

$$= x_1 x_2 x_3 x_4 x_5$$

$$f^{8/0} = \overline{\overline{x_1 x_2 + x_3 x_4}} = x_1 x_2 \cdot \overline{x_3 x_4} = x_1 x_2 (\overline{x_3} + \overline{x_4})$$

$$F^{8/0} = x_1 x_2 \overline{x_3} x_4 x_5 \oplus (x_1 x_2 \overline{x_3} + x_1 x_2 \overline{x_4})$$


$$= x_1 x_2 \overline{x_3} x_4 x_5 \cdot \overline{(x_1 x_2 \overline{x_3} + x_1 x_2 \overline{x_4})} + x_1 x_2 \overline{x_3} x_4 x_5 \cdot (x_1 x_2 \overline{x_3} + x_1 x_2 \overline{x_4})$$

$$= x_1 x_2 \overline{x_3} x_4 + x_1 \overline{x_3} x_2 x_4 + x_1 x_2 \overline{x_4} + x_1 \overline{x_3} x_2 x_5 + x_1 \overline{x_5} x_2 x_4$$

$$= x_1 x_2 x_4 + x_1 \overline{x_3} x_2 x_5$$

The tests are 11000, 11100, 11001, 11101 and 11010

- Let us use z to denote the fault

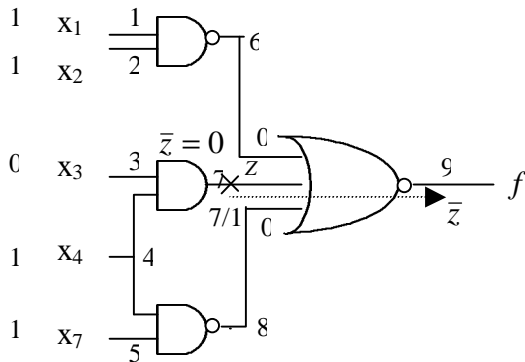

The test is 11011