

# Introduction to LTspice

Dr. Vahe Caliskan

*Department of Electrical and Computer Engineering*

vahe@uic.edu

<http://www.uic.edu/~vahe>



# Agenda

---

- ▶ Purpose of Presentation
- ▶ What is spice? What is LTspice? What can LTspice do for me?
- ▶ LTspice features / Running LTspice / User Interface
- ▶ LTspice Analyses
  - ▶ DC Operating Point and DC Sweep Analysis
  - ▶ Transient Analysis, Fourier, FFT
  - ▶ AC Small-Signal Analysis
  - ▶ Parameter Sweep Analysis
  - ▶ Monte-Carlo & Worst-Case Analysis
- ▶ Incorporating 3<sup>rd</sup> Party information (models, subcircuits)
- ▶ Implementing Hierarchies
- ▶ Questions / Comments

# What is the purpose of this presentation?

---

- ▶ To introduce/familiarize you with LTspice (spice)
  - ▶ Many already familiar with PSpice w/Schematics or Multisim
- ▶ Demonstrate simulator capabilities that might be of use to your work
  - ▶ Even crude analyses in early design stages are beneficial
  - ▶ Laboratory pre-labs can be performed using a simulator
  - ▶ Most homework assignments can be validated using a simulator
- ▶ Open dialogue in the general area of modeling/simulation
- ▶ My purpose is NOT to sell/promote Linear Tech ICs
  - ▶ I do not own LTC stock ☹

# What is spice?

---

- 1972 SPICE 1 (Simulation Program with Integrated Circuit Emphasis)
- 1975 SPICE 2 (L. Nagel's Ph.D. thesis is the user guide)
- 1983 SPICE 2G6
- 1985 SPICE 3
- 1993 SPICE 3F4
- 1996  $\mu$ Power SwitcherCAD (simulation based)
- 1999 LTspice/SwitcherCAD III (SPICE based)
- 2004 500,000 base LTspice downloads
- 2009 LTspice IV (multi-processor), > 1 million downloads

# What is LTspice?

---

- ▶ Rewrite of Berkeley SPICE 3F4/5
  - ▶ Reduced address calculation and function calling overhead
  - ▶ Improved timestep control and numerical methods
  - ▶ Enhanced integration methods and convergence improvements
  - ▶ Alternate solver/SPARSE matrix package 1000× more accurate
  - ▶ Circuit size limited by computer memory
- ▶ Added/Enhanced semiconductor models
  - ▶ Diode recombination current
  - ▶ JFET impact ionization current
  - ▶ BJT quasi-saturation
  - ▶ VBIC
  - ▶ Binned BSIM3v3.2.4, BSIM4.4.0, BSIMSOI3.2
  - ▶ VDMOS (a new vertical double diffused MOSFET for power MOS)
  - ▶ EKV 2.6

# What can LTspice do for me?

---

- ▶ General circuit simulation with an unlimited, high-performance SPICE
  - ▶ Free download of the software is the full version (no restrictions)
  - ▶ No node limitations
  - ▶ Much fewer “convergence” issues
  - ▶ Already being used by many students at UIC
  - ▶ The price is right! Performance/cost ratio is  $\infty$
  - ▶ It’s good, cheap and fast! 😊
- ▶ Simulate switch-mode power supply and associated circuitry
  - ▶ Model of nearly every IC manufactured by Linear
  - ▶ Example simulations for nearly every IC from Linear
    - ▶ These are normally the “typical application” shown page 1 of datasheet
    - ▶ This is the quickest way to get started with SMPS design

# LTspice Features

---

- ▶ General purpose schematic capture
  - ▶ Unlimited schematic size
  - ▶ Unlimited depth of hierarchy
  - ▶ Symbol editor
  - ▶ Complete documentation
  
- ▶ Integrated with Industry superlative SPICE simulator
  - ▶ Unlimited, professional-quality SPICE proven for IC design
  - ▶ Unmatched combination of robustness, accuracy, speed and compatibility
  - ▶ Advanced analysis/simulation options, parameter sweeps, FFTs, etc.
  - ▶ Run 3rd party models
  - ▶ Active independent users' groups (Yahoo groups)

# Two ways to run LTspice


---

- ▶ Schematic editor is usually used to enter the circuit information
  - ▶ Component selected from parts list
  - ▶ Wiring of circuit
  - ▶ Choosing type of analysis
  - ▶ Running simulation
  - ▶ Post-processing of results (viewing and analyzing waveforms)
- ▶ Direct simulation of netlist files and batch-mode simulation also available
  - ▶ Circuit is in the form of a netlist (text input, no schematic)
  - ▶ Running simulation, analysis and post-processing is identical

**Demonstration**



# LTspice User Interface

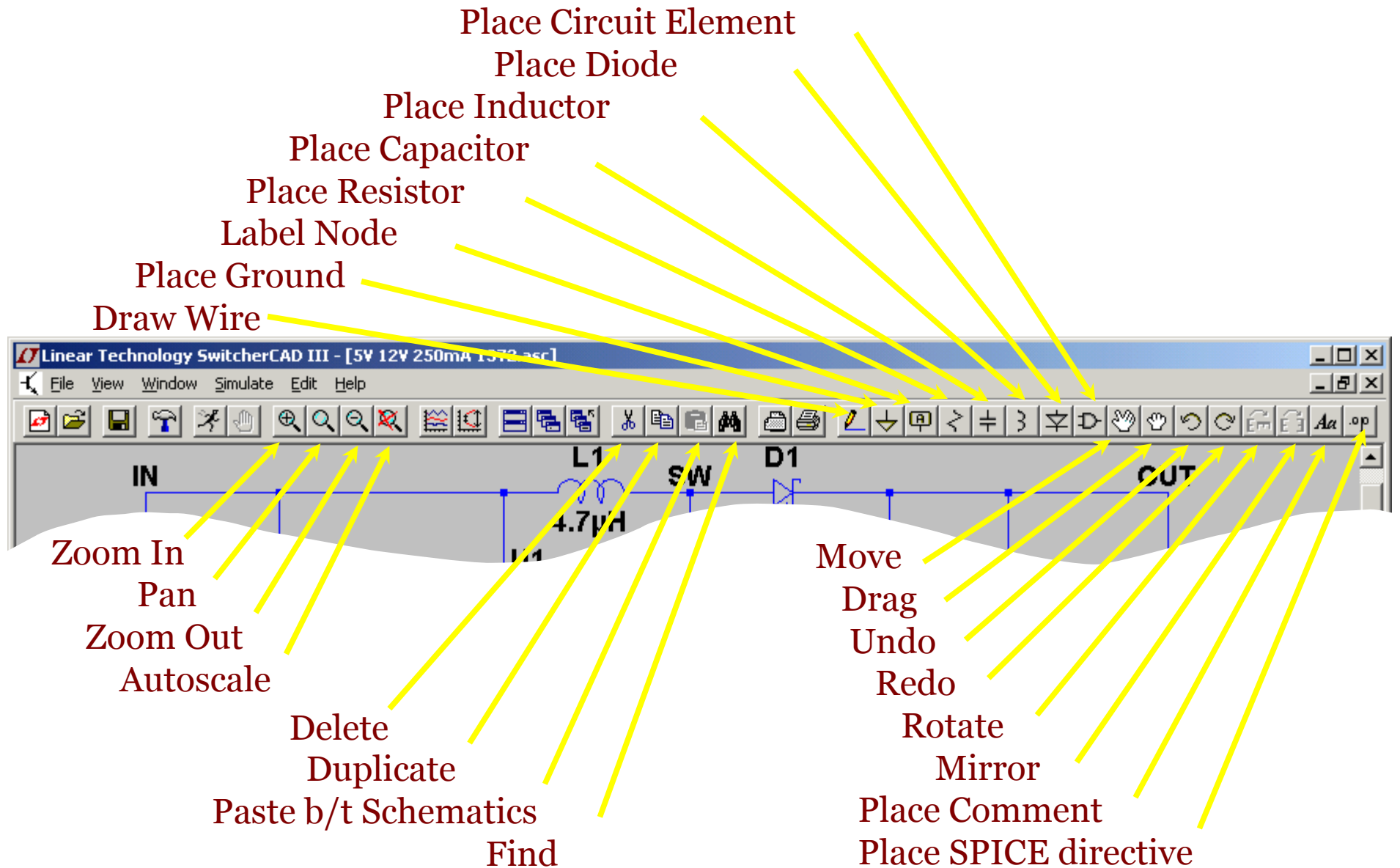

# DC Operation Point Analysis (.op)

---

- ▶ Solve for system variables assuming equilibrium ( $d/dt \rightarrow 0$ )
  - ▶ Capacitors  $\rightarrow$  open-circuit
  - ▶ Inductors  $\rightarrow$  short-circuit
- ▶ Operating point results given in textual form
  - ▶ Node voltages may also be displayed after a `.op` run
- ▶ Newton-Raphson method is used for nonlinear systems

Demonstration

# Useful Features

---

- ▶ Frequently used parameters can be defined using a `.param` statement
  - ▶ `.param fs=10kHz, Ts={1/fs}`
- ▶ User-defined functions declared using the `.func` (`.function`) statement
  - ▶ `.func myfunc(f1,f2) (f1+f2-f1*f2)`
- ▶ Fourier Analysis using `.four` statement (used with `.tran`)
  - ▶ `.four 2kHz v(out)`
- ▶ FFT available directly from Waveform Viewer

Demonstration

# DC Sweep Analysis (`.dc`)

---

- ▶ Very similar to DC Operating Point Analysis
- ▶ Basically an `.op` analysis where one (or more) dc sources are varied
- ▶ Up to three sources may be “swept”
- ▶ DC Sweep results reported in plot
- ▶ Special dc sweep → `.temp`

Demonstration

# Transient Analysis (.tran)

---

- ▶ Nonlinear time-domain analysis
- ▶ Most utilized analysis and the one that produces most difficulties
- ▶ Simulation problems can often be resolved by ...
  - ▶ Using more realistic (non-ideal) models
  - ▶ Addition of parasitic elements not on ideal schematic
  - ▶ Adjusting simulator settings (integration method, error tolerance, etc.)
  - ▶ Developing your own models
  - ▶ Not using PSpice ☺
- ▶ Fourier Analysis and FFT available after running transient analysis

**Demonstration**

# AC Small-Signal Analysis (.ac)

---

- ▶ Simulation of linearized system to ac excitation
- ▶ Linearization around operating point from .op analysis
  - ▶ Actually an .op analysis is always run before any of the other analyses
- ▶ Linearized system simulation valid if excitation is “small”
- ▶ AC Analysis usually runs quite fast since models are already linearized

Demonstration

# Parameter Sweep Analysis (`.step`)

---

- ▶ Any parameter declared with a `.param` statement can be used with `.step`
- ▶ Using `.step` will run the chosen analysis (`.tran`, `.ac`, etc.) multiple times
- ▶ The actual stepping can be linear, logarithmic or given by a list

Demonstration

# Monte Carlo & Worst-Case Analysis

---

- ▶ Main idea is to run an analysis (`.tran`, `.ac`, etc.) multiple times with
  - ▶ Gaussian (normal) distribution
  - ▶ Worst-Case distribution
  - ▶ Analysis: `.step param run 1 1000 1` (`run=1` is nominal case)
  
- ▶ Custom functions make these analyses a bit easier
  - ▶ `.function normal(nom,tol) nom*(1+gauss(tol/3))`
  - ▶ `.function wc(nom,tol) if(flat(0.5)+0.5,nom*(1+tol),nom*(1-tol))`
  - ▶ `.function normal(nom,tol) if(run==1, nom, nom*(1+gauss(tol/3)))`
  - ▶ `.function wc(nom,tol) if(run==1, nom, if(flat(0.5)>0,nom*(1+tol),nom*(1-tol)))`

Demonstration



# Importing Models, Creating Symbols

---

- ▶ Multiple ways of importing models (`.model`) and subcircuits (`.subckt`)
  - ▶ Place model/subcircuit text directly on schematic
  - ▶ Place model/subcircuit text in files, then use (`.inc <file>`)
- ▶ Main parts databases can also be updated
- ▶ Creating a symbol is pretty easy
  - ▶ Use already existing symbols unless a special symbol is necessary

Demonstration

# Hierarchical Modeling

---

- ▶ Hierarchical schematic drafting has powerful advantages
- ▶ Larger circuits can be drafted while retaining clarity of smaller schematics
- ▶ Repeated circuitry to be easily handled in an abstract manner
- ▶ Blocks of circuitry can be stored in libraries for later use different projects

Demonstration

# Model Parameter Stepping

---

- ▶ How do we handle stepping a device parameter? (e.g. BJT  $\beta$ )
- ▶ Be sure to understand **all** device parameters before doing this
- ▶ Stepping can easily be done by setting device parameter using `.param`
- ▶ Then simply use `.step` with you choice of analysis (e.g. MC, WC)

Demonstration

# BJT dc Model

---

- ▶ Custom BJT hierarchical model used for dc analysis
- ▶ Input parameters:  $\beta_F$ ,  $\beta_R$ ,  $V_{BE,on}$ ,  $V_{BC,on}$
- ▶ Model automatically determines mode
  - ▶ cutoff, saturation, forward active, reverse active
- ▶ Works great on ECE 340 homework problems 😊

Demonstration

# MOSFET dc Model

---

- ▶ Custom MOSFET hierarchical model used for dc analysis
- ▶ Input parameters:  $K$  and  $V_t$
- ▶ Model also determines mode (cutoff, ohmic, saturation)
- ▶ Works great on ECE 340 homework problems 😊

Demonstration

# Filter Analysis / Bode Plots

---

- ▶ Circuits based on op-amp (ideal or non-ideal)
- ▶ Pure s-domain expressions are also allowed
- ▶ Custom blocks can determine asymptotic Bode plots
- ▶ Works great on ECE 342 / ECE 412 homework problems

Demonstration

# Step Response, Laplace Transforms, FFT

---

- ▶ ECE 310/350 (step response, Laplace transforms, etc.)
- ▶ ECE 311/411 (FFT)

Demonstration

# LTspice Resources

---

- ▶ LTspice (free download)

- ▶ <http://ltspice.linear.com/software/LTspiceIV.exe>

- ▶ LTspice Getting Started Guide

- ▶ <http://ltspice.linear.com/software/LTspiceGettingStartedGuide.pdf>

- ▶ LTspice User's Guide

- ▶ <http://ltspice.linear.com/software/scad3.pdf>

- ▶ LTspice Users' Group (free — registration required)

- ▶ <http://tech.groups.yahoo.com/group/LTspice/>

- ▶ LTspice Users' Group Documentation (free — registration required)

- ▶ <http://tech.groups.yahoo.com/group/LTspiceDocs/>